

Verification Plan: 4 bit Alu

1.DUT Overview

The DUT is a 4bit ALU with no clk or reset signals, which performs arithmetic and logic operations on 2 input operands. Which operation is performed gets decided based on a selector input.

The RTL implementation is a black box, Verification is based solely on the given design specification

Signal	Direction	Width	Description
A	Input	4bit	Operand A
B	Input	4bit	Operand B
op	Input	3bit	Operation Selector
carry	Output	1bit	Carry(add/sub)or 0 for logic ops
Y	Output	4bit	ALU result

Opcode (op)	Operation	Description	Example (A=3, B=2)	Y	carry
000	ADD	$Y = A + B$	$3 + 2$	0101	Carry = 0
001	SUB	$Y = A - B$ (two's complement)	$3 - 2$	0001	Carry = 0
010	AND	Bitwise AND	$3 \& 2$	0010	0
011	OR	Bitwise OR	$3 2$	0011	0
100	XOR	Bitwise XOR	$3 \wedge 2$	0001	0
101	NOT A	Bitwise negation of A	~ 3	1100	0
110	PASS A	Output A	3	0011	0
111	PASS B	Output B	2	0010	0

2.Verification Objectives

- Verify Carry is set correctly for Add/Sub and forced to 0 for rest
- Verify Y output for all 8 operations across all input combination
- All possible opcodes are defined so no verification for faulty opcode needed

3.Features to Verify

Feature	Test
ADD: $Y = A + B$ (4bits)	All A,B combinations
ADD: carry = MSB of 5bit sum	All A,B combinations
SUB: $Y = A - B \text{ mod } 16$	All A,B combinations
SUB: Carry bit	All A,B combinations
AND/OR/XOR/NOT: Correct Y	All A,B combinations
PASS A: $Y = A$	All A,B combinations
PASS B: $Y = B$	All A,B combinations
INVALID OPCODE: $Y = 0$, Carry=0	None - all 8 opcodes possible are mapped

4.Testbench Architecture

1. Simple behavioral reference model implemented in SystemVerilog based on design specifications to predict expected value
2. Nested for loops iteration over opcodes and A, B operands feed both refrence model and DUT
3. Outputs get compared directly - Mismatches categorized in:
 - a. Y mismatch,
 - b. Carry mismatch
 - c. Y & Carry mismatch
4. Per-opcode, reports Mismatches per category. If opcodes has mismatches displays all operands and corresponding Y and carry outputs categorized in Passing and Failing

5.Coverage Goals

Since the design is small enough we aim for a 100% coverage:

Input Space: $8 \text{ ops} * 16 \text{ A} * 16 \text{ B} = 2048$ test iterations

6.Tools

- Simulator: QuestaSim / ModelSim
- Language: SystemVerilog
- Waveform viewer: QuestaSim wave viewer (for the ADD waveform deliverable)
- VCD dump: for waveform capture

Results & Report

CODE

```
`timescale 1ns/1ps

module alu_compare_4bit (
    input  [2:0] op,
    input  [3:0] A,
    input  [3:0] B,
    output reg [3:0] Y,
    output reg      carry
);

    always @(*) begin
        case (op)
            3'b000: {carry, Y} = A + B;
            3'b001: {carry, Y} = A - B;
            3'b010: {carry, Y} = {1'b0, A & B};
            3'b011: {carry, Y} = {1'b0, A | B};
            3'b100: {carry, Y} = {1'b0, A ^ B};
            3'b101: {carry, Y} = {1'b0, ~A};
            3'b110: {carry, Y} = {1'b0, A};
            3'b111: {carry, Y} = {1'b0, B};
            default: {carry, Y} = 5'b00000;
        endcase
    end

endmodule

module alu_4bit_tb;

    reg  [2:0] _op;
    reg  [3:0] _A;
    reg  [3:0] _B;

    wire [3:0] _Y;
    wire      _carry;
```

```

wire [3:0] _Y_cmp;
wire      _carry_cmp;

integer op_i, a, b;
integer i;
integer errors;

integer y_mismatch      [0:7];
integer carry_mismatch  [0:7];
integer joined_mismatch [0:7];

reg [63:0] op_name;

alu_4bit dut (
    .A(_A),
    .B(_B),
    .op(_op),
    .Y(_Y),
    .carry(_carry)
);

alu_compare_4bit ref_model (
    .A(_A),
    .B(_B),
    .op(_op),
    .Y(_Y_cmp),
    .carry(_carry_cmp)
);

initial begin
    $dumpfile("alu_4bit.vcd");
    $dumpvars(0, alu_4bit_tb);

    errors = 0;

    for (i = 0; i < 8; i = i + 1) begin
        y_mismatch[i]      = 0;
        carry_mismatch[i]  = 0;
        joined_mismatch[i] = 0;
    end
end

```

```

for (op_i = 0; op_i < 8; op_i = op_i + 1) begin
    case (op_i)
        0: op_name = "ADD";
        1: op_name = "SUB";
        2: op_name = "AND";
        3: op_name = "OR";
        4: op_name = "XOR";
        5: op_name = "NOT A";
        6: op_name = "PASS A";
        7: op_name = "PASS B";
    endcase

    $display("\n----- %s (%03b) -----", op_name, op_i[2:0]);

    // Pass 1: print all FAILs
    for (a = 0; a < 16; a = a + 1) begin
        for (b = 0; b < 16; b = b + 1) begin
            _op = op_i[2:0];
            _A = a[3:0];
            _B = b[3:0];

            #1;

            if ((_Y !== _Y_cmp) || (_carry !== _carry_cmp)) begin
                errors = errors + 1;

                if ((_Y !== _Y_cmp) && (_carry !== _carry_cmp)) begin
                    joined_mismatch[op_i] = joined_mismatch[op_i] + 1;
                    $display("FAIL (Y+carry) A=%b B=%b -> DUT: Y=%b carry=%b
Ref: Y=%b carry=%b",
                        _A, _B, _Y, _carry, _Y_cmp, _carry_cmp);
                end
                else if (_Y !== _Y_cmp) begin
                    y_mismatch[op_i] = y_mismatch[op_i] + 1;
                    $display("FAIL (Y only) A=%b B=%b -> DUT: Y=%b
Ref: Y=%b",
                        _A, _B, _Y, _Y_cmp);
                end
                else begin
                    carry_mismatch[op_i] = carry_mismatch[op_i] + 1;
                    $display("FAIL (carry) A=%b B=%b -> DUT: carry=%b
Ref: carry=%b Y=%b",

```

```

        _A, _B, _carry, _carry_cmp, _Y);
    end
end
end
end

// Pass 2: if this opcode had errors, print all PASSes
if (y_mismatch[op_i] + carry_mismatch[op_i] + joined_mismatch[op_i] > 0)
begin
    $display("--- Correct combinations ---");
    for (a = 0; a < 16; a = a + 1) begin
        for (b = 0; b < 16; b = b + 1) begin
            _op = op_i[2:0];
            _A = a[3:0];
            _B = b[3:0];

            #1;

            if ((_Y === _Y_cmp) && (_carry === _carry_cmp)) begin
                $display("PASS          A=%b B=%b -> Y=%b carry=%b",
                    _A, _B, _Y, _carry);
            end
        end
    end
end
end
end

if (errors == 0) begin
    $display("All combinations matched.");
end
else begin
    $display("\n===== FINAL SUMMARY =====\n");

    for (i = 0; i < 8; i = i + 1) begin
        case (i)
            0: op_name = "Add";
            1: op_name = "Sub";
            2: op_name = "AND";
            3: op_name = "OR";
            4: op_name = "XOR";
            5: op_name = "NOT A";
            6: op_name = "PASS A";

```

```

        7: op_name = "PASS B";
    endcase

    $display("%s (%03b) :", op_name, i[2:0]);
    $display("Y mismatch      : %0d", y_mismatch[i]);
    $display("Carry mismatch   : %0d", carry_mismatch[i]);
    $display("Joined mismatch : %0d\n", joined_mismatch[i]);
end

    $display("Total mismatches: %0d", errors);
end


$finish;
end

endmodule

```


It's a total of 2048 tests - all possible combinations of inputs get tested. This gives me full coverage. As the module is very small such extensive testing does not run into any time issues.

Waveforms

 

Waveform of alu_4bit_v1. As visible the Pattern for Y and Y_cmp aswell as carry and carry_cmp are identical which matches the tb report of no mismatches between the DUT and

the reference model.

 

Waveform of alu_4bit_v5. Here the cmp and corresponding DUT signals do not match. This is consistent with the tb reporting that all adds mismatched with the reference outputs (failed the test) for this DUT version.

Results

Version	Failed Ops	Reason for Failure
v0	None	—
v1	None	—
v2	Sub	Carry not working for negative numbers ($B > A$)
v3	Or & And	Or behaves like And And behave like Or -> Opcode wrongly set
V4	None	—
V5	Xor, Add	Xor: 0 xor 0 results in 1 instead of 0 Add: +1 off the correct results

Side Notes

Time spent outside the Lab: 1.5 - 2h

AI usage :

Model: Claude code

Prompts (paraphrased) :

1. Clean Up the tb (clean up set in global claude context to not touch logic -> linting)
-> added spacing, correct indents etc. Kinda exactly what a good linting program would do
2. Make the print statements prettier
-> Adds Nicer formatted Headers, better description etc (e.g. see Final Summary print statement)
3. Add Print statements to also printing correct combinations if opcode has some failed combinations
-> added logic for printing correct combinations